

Lab 7 Report

ECE 4525

Mack Usmanova

Jena Francis

10/22/25

Introduction.....	3
Procedure .....	4
Task One:.....	4
Task Two:.....	9
Task Three:.....	12
Conclusion .....	16
Appendix .....	17
Task One .....	17
Task Two .....	20
Task Three.....	23

# Introduction

The purpose of this lab was to design and implement a controller for a DRAM chip using VHDL. The main goal of this lab was to design a controller that can execute both read and write operations for a DRAM chip while meeting its AC timing specifications. The first task involved developing VHDL code to control a simple read cycle. We ensured the DRAM control signals were correctly generated, and timing constraints were verified through post-route simulation and the oscilloscope. The second task was similar but instead of a read cycle we developed a write cycle. Again, timing constraints were verified through post-route simulation and the oscilloscope. Lastly, task three involved integrating both read and write operations into one. Overall, this lab provided valuable experience in timing diagrams and DRAM implementation.

# Procedure

## Task One:

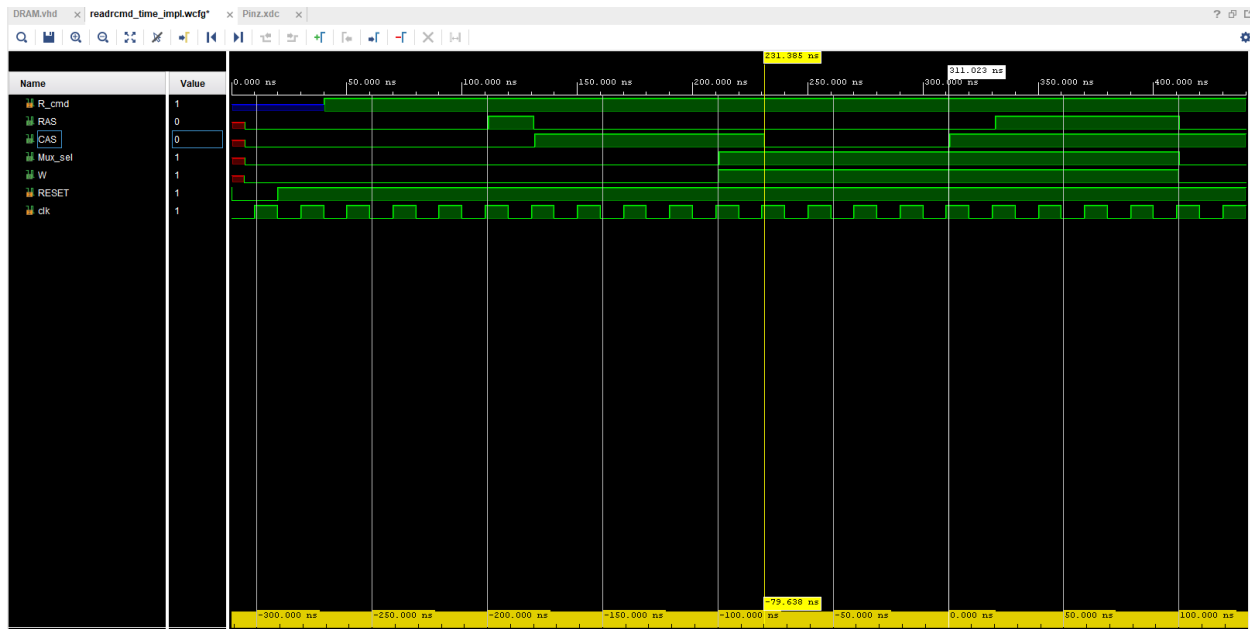


Figure 1: shows the post implementation timing simulation for task 1. the outputs are delayed until 110ns is reached and the rest of the output matches the desired output given in the datasheet.

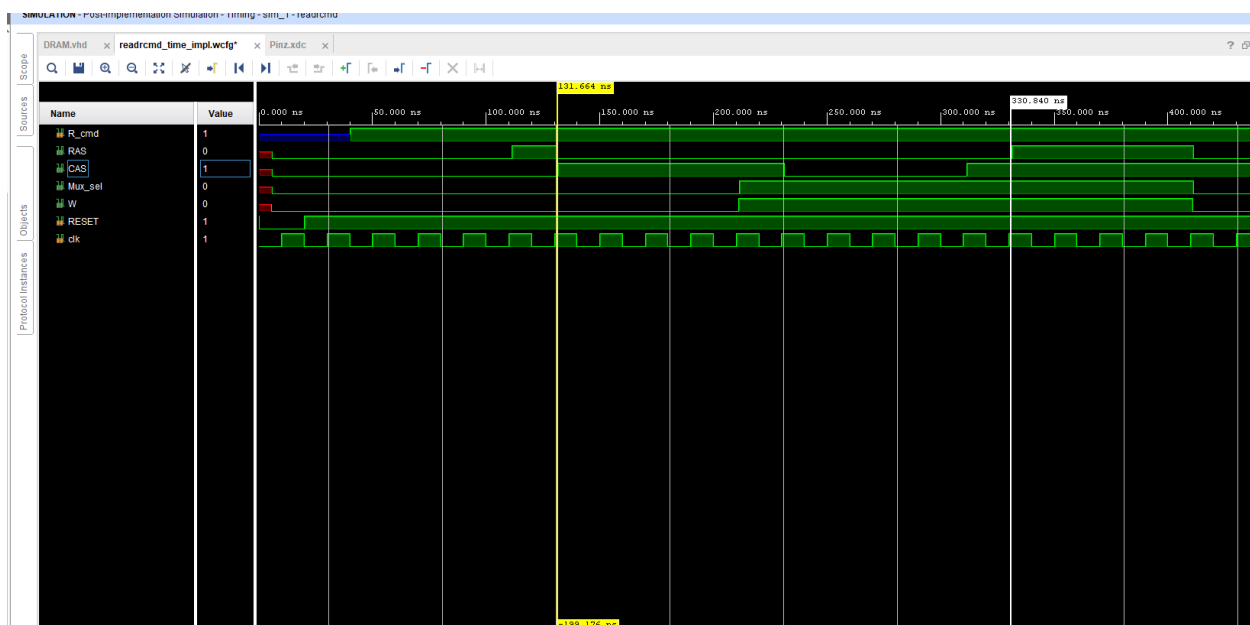


Figure 2: the minimum for  $t_{RAS}$  is 70ns and max is 10,000ns, we have 199.176 which is in between the limit.

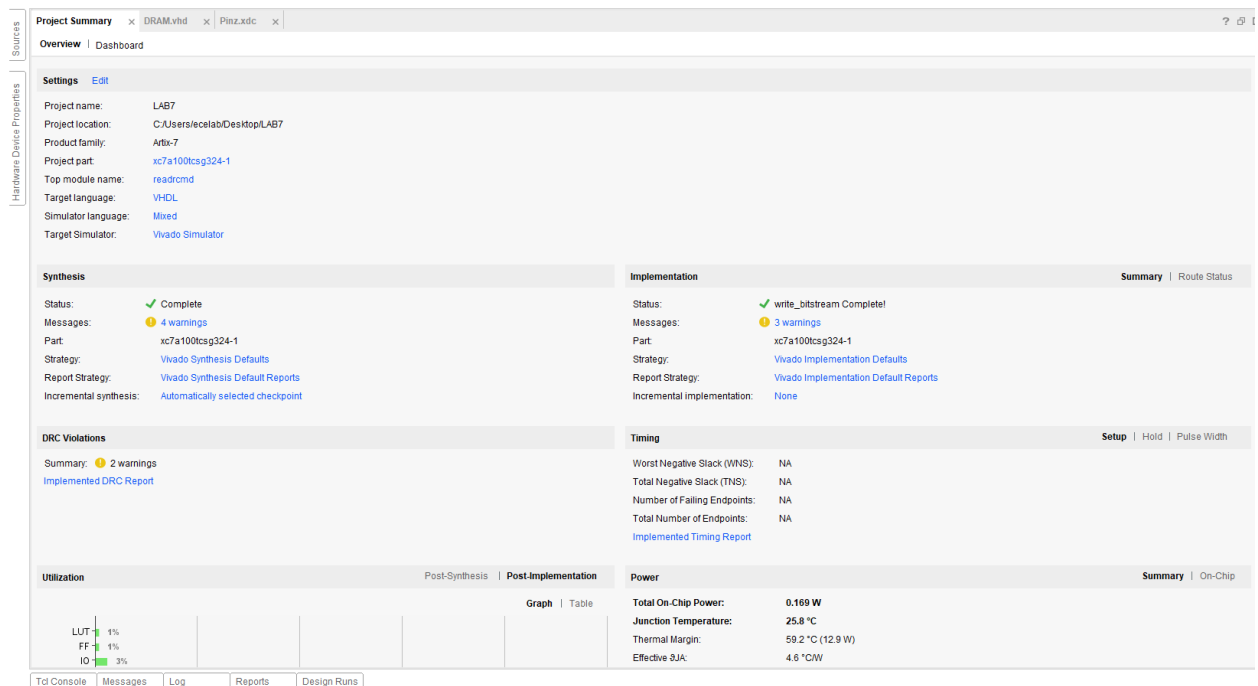


Fig 3: This is the project summary page for task one.

 


Fig 4: This is the oscilloscope view. D4 is Mux\_sel, D3 is CAS, D2 is RAS, D1 is W and D0 is the clk.

MSO-X 3034A, MY53480232: Thu Oct 23 09:44:58 2025

 


Fig 5: This is the oscilloscope view. D<sub>4</sub> is Mux\_sel, D<sub>3</sub> is CAS, D<sub>2</sub> is RAS, D<sub>1</sub> is W and D<sub>0</sub> is the clk.

MSO-X 3034A, MY53480232: Thu Oct 23 09:47:00 2025

 


Figure 6: This is the oscilloscope view. D1 is Mux\_sel, D2 is CAS, D3 is RAS, D4 is W and D0 is the clk. The outlined timeline above shows how long RAS stayed low for which as mentioned above, the max limit is 10,000ns

MSO-X 3034A, MY53480232: Thu Oct 23 09:47:30 2025

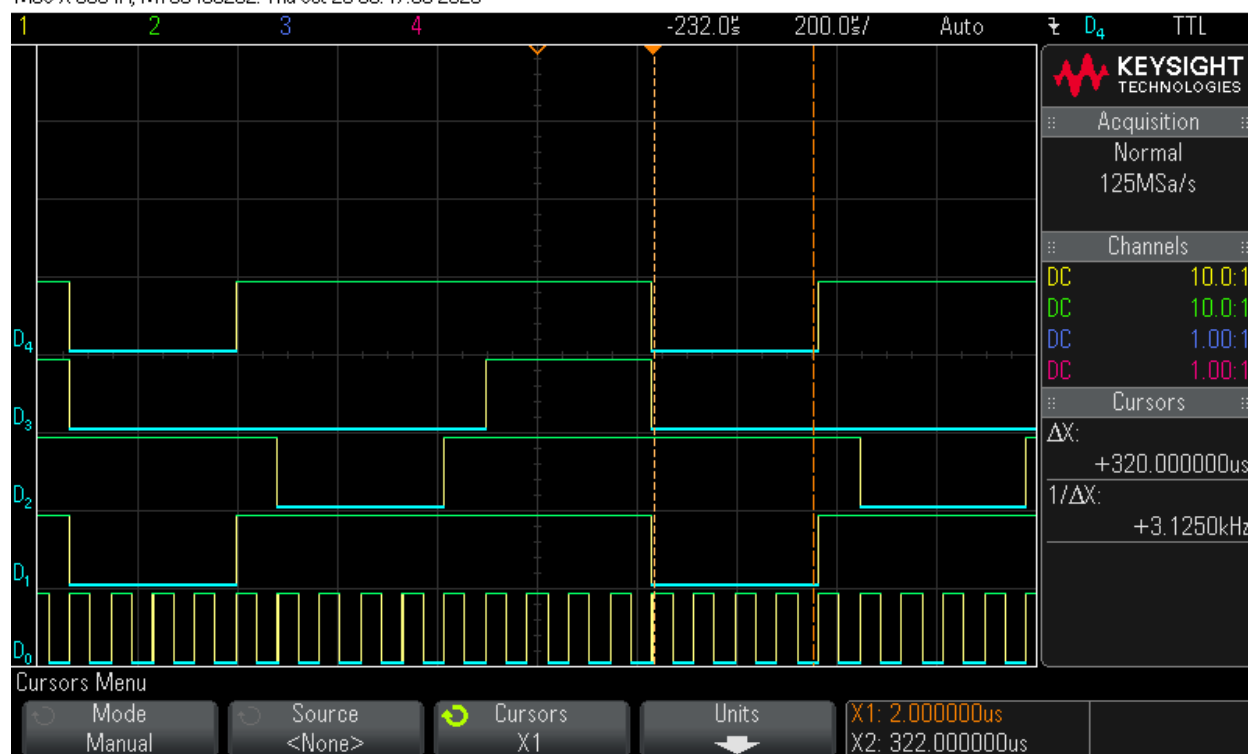


Figure 7: the outlined timeline above displays how long it took for column address to be selected by mux\_sel and how long it too for write to be enabled.



## Task Two:

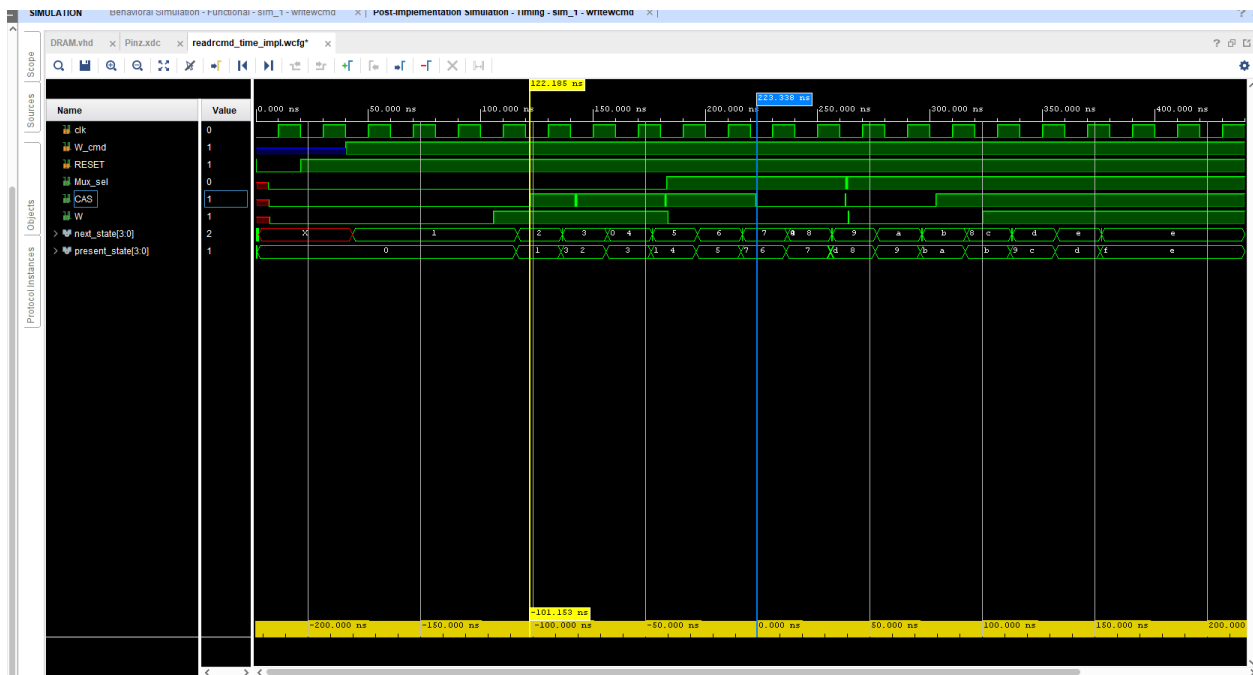


Figure 8: the outlined timeline displayed above shows  $t_{RCD}+t_{CRP}$  the minimum of which seems to be 25 plus some missing nanoseconds and the maximum is undefined

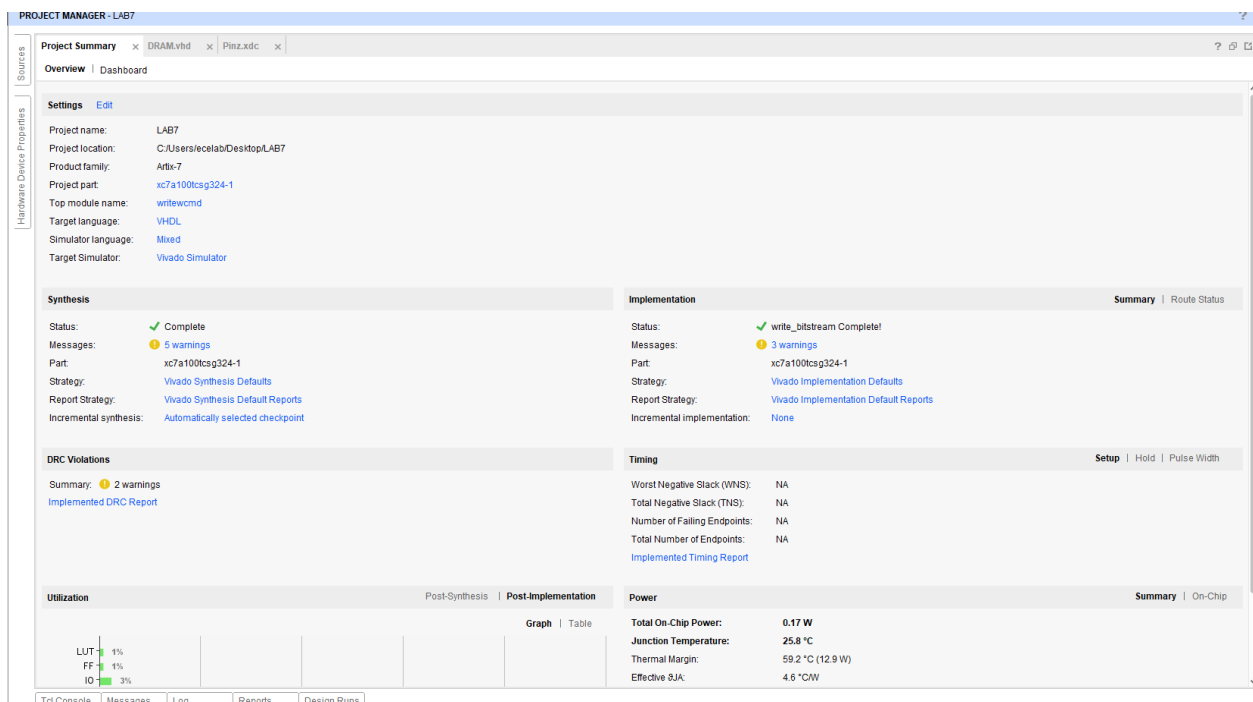


Fig 9: this is the project summary report for task two.

MSO-X 3034A, MY53480232: Thu Oct 23 10:25:58 2025

 


Fig 10: This is the oscilloscope view. D1 is Mux\_sel, D2 is CAS, D3 is RAS, D4 is W and D0 is the clk.

MSO-X 3034A, MY53480232: Thu Oct 23 10:25:46 2025

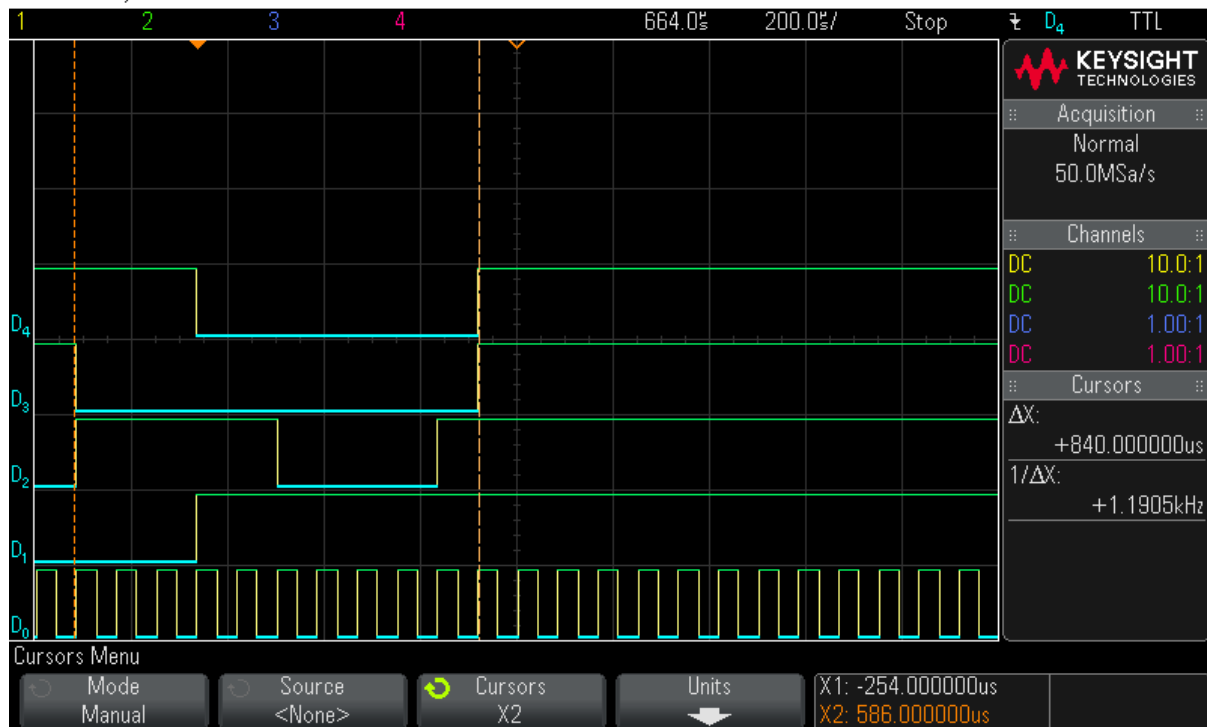


Figure 11: This is the oscilloscope view. D1 is Mux\_sel, D2 is CAS, D3 is RAS, D4 is W and D0 is the clk.

MSO-X 3034A, MY53480232: Thu Oct 23 10:26:28 2025

 


Figure 12: This is the oscilloscope view. D1 is Mux\_sel, D2 is CAS, D3 is RAS, D4 is W and D0 is the clk.

## Task Three:

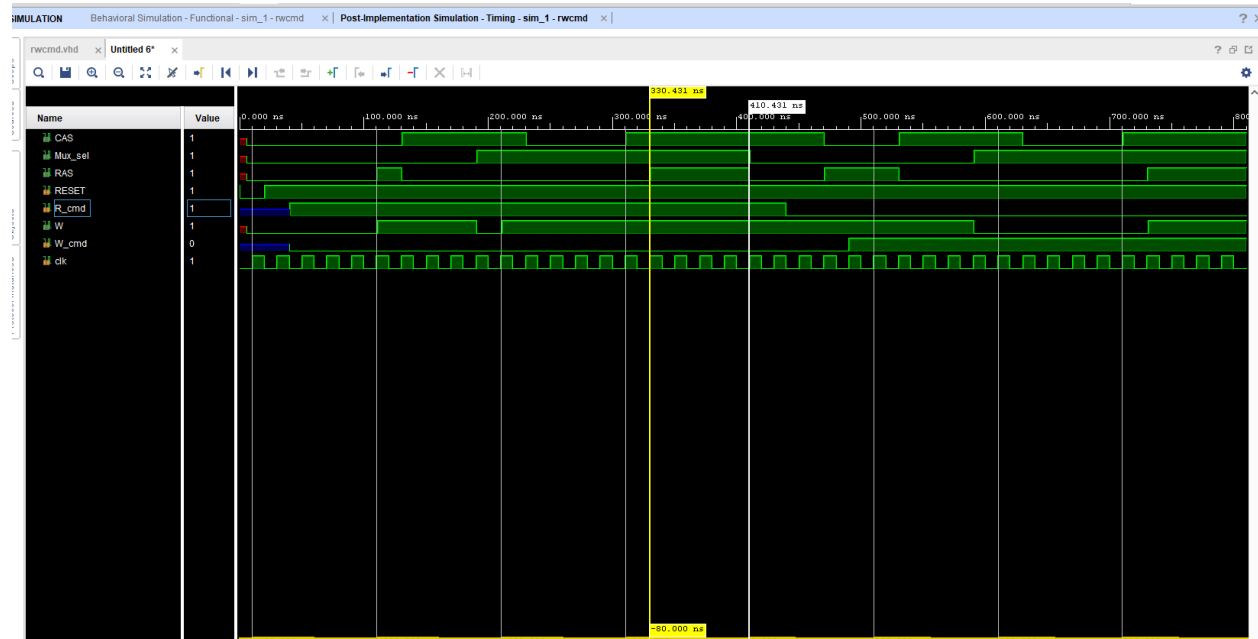


Figure 13: the post implementation timing simulation above has the  $t_{rp}$  outlined for which the minimum is 50ns and max is undefined. We have 80ns.

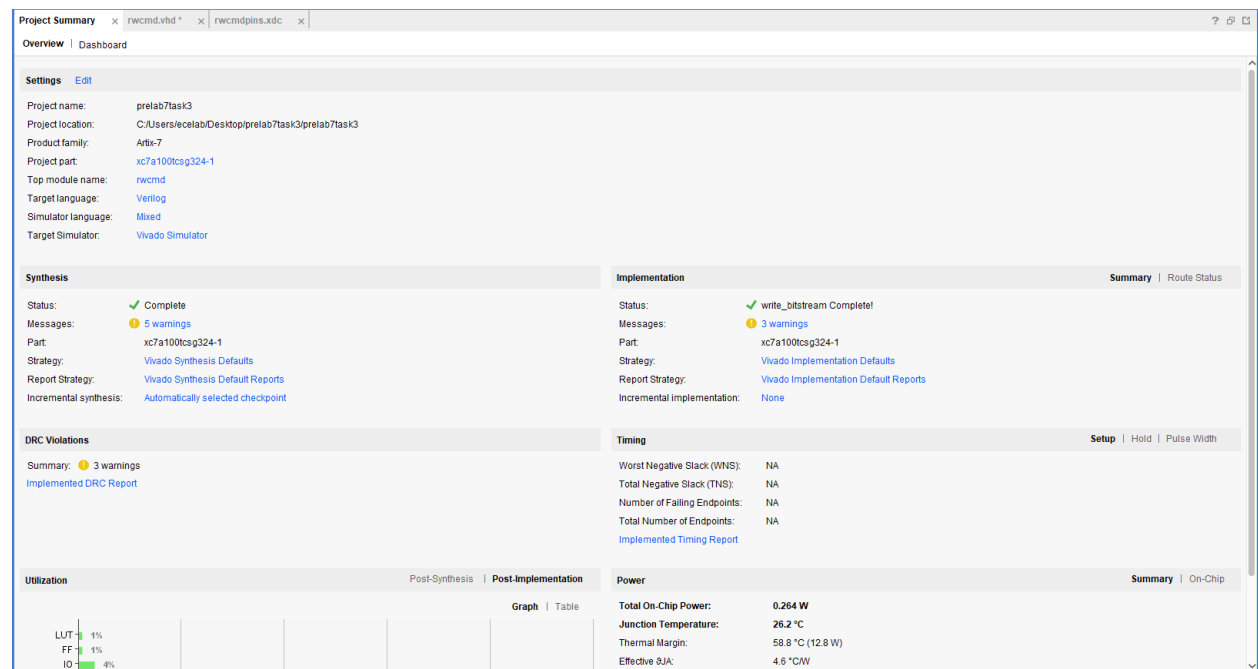


Fig 14: this shows the project summary report for task three.

MSO-X 3034A, MY53480232: Thu Oct 23 10:50:12 2025

 


Fig 15: This is the oscilloscope view. D1 is Mux\_sel, D2 is CAS, D3 is RAS, D4 is W and D0 is the clk.

MSO-X 3034A, MY53480232: Thu Oct 23 10:50:32 2025

 


Figure 16: This is the oscilloscope view. D4 is Mux\_sel, D3 is CAS, D2 is RAS, D1 is W and D0 is the clk.

1 2 3 4 666.0ns 200.0MS/s Auto

**KEYSIGHT TECHNOLOGIES**

Acquisition  
Normal  
125MSa/s

Channels  
DC 10.0:1  
DC 10.0:1  
DC 1.00:1  
DC 1.00:1

Cursors  
 $\Delta X$ : +350.000000us  
 $1/\Delta X$ : +2.8571kHz

Cursors Menu  
Mode Manual  
Source <None>  
Cursors X1  
Units  
X1: 154.000000us  
X2: 504.000000us

Figure 18: shows the schematic for task 3, there was no need for a schematic in lab report therefore we voluntarily provided it for task3 only where la stands for logic analyzer and wg for wave generator.

## Conclusion

In the lab, the design and implementation of a DRAM controller provided practical knowledge of synchronous sequential circuit design and finite state machines. Task one involved creating a VHDL code for a simple read cycle for the DRAM chip. For task two, we implemented a write cycle for the DRAM chip. In task three, both read and write operations were integrated into a single DRAM controller. Simulations and the oscilloscope verified that the state machine successfully generated the proper signal transitions for each task. In conclusion, this lab helped reinforce key skills in digital design and memory interface development.



# Appendix

## Task One

Vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity readrcmd is
    Port (
        clk, R_cmd, RESET: in std_logic;
        Mux_sel, CAS, RAS, W: out std_logic
    );
end readrcmd;

architecture Behavioral of readrcmd is
    type state is (idle,s1,s2,s3,s4,s5,s6,s7,s8,s9,s10,s11,s12,s13,s14);
    signal present_state, next_state: state:= idle;
begin
    process(R_cmd, present_state)
    begin
        case present_state is
            when idle =>
                CAS <= '0';
                RAS <= '1';
                W <= '0';
                Mux_sel <= '0';
                if R_cmd = '1' then
                    next_state <= s1;
                else
                    next_state <= idle;
                end if;

            when s1 =>
                CAS <= '1';
                RAS <= '0';
                W <= '0';
                Mux_sel <= '0';
                next_state <= s2;

            when s2 =>
                CAS <= '1';
                RAS <= '0';
                W <= '0';
                Mux_sel <= '0';
                next_state <= s3;

            when s3 =>
                CAS <= '1';
                RAS <= '0';
                W <= '0';
                Mux_sel <= '0';
                next_state <= s4;

            when s4 =>
```

```
Mux_sel <= '0';
CAS <= '1';
RAS <= '0';
W <= '0';
next_state <= s5;

when s5 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '0';
W <= '1';
next_state <= s6;

when s6 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s7;

when s7 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s8;

when s8 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s9;

when s9 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s10;

when s10 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '0';
W <= '1';
next_state <= s11;

when s11 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
next_state <= s12;

when s12 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
next_state <= s13;

when s13 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
next_state <= s14;

when s14 =>
Mux_sel <= '1';
```

```

CAS <= '1';
RAS <= '1';
W <= '1';
if R_cmd = '1' then
    next_state <= s1;
else
    next_state <= idle;
end if;

when others =>
    next_state <= idle;

end case;
end process;

process
begin
wait until clk'event and clk = '1';
    if reset <= '0' then
        present_state <= idle;
    else
        present_state <= next_state;
    end if;
end process;

end Behavioral;

```

## Tcl

```

restart
add_force clk {0 0ns} {1 10ns} -repeat_every 20ns

add_force RESET {0 0ns}
run 20ns
add_force RESET {1 0ns}
run 20ns
add_force R_cmd {1 0ns}
run 300ns

```

## Xdc

```

## Clock signal
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk]

#set_property -dict { PACKAGE_PIN E3 IOSTANDARD LVCMOS33 } [get_ports { CLK100MHZ }];
#IO_L12P_T1_MRCC_35 Sch=clk100mhz

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK100MHZ}];

##Buttons
set_property -dict { PACKAGE_PIN C12 IOSTANDARD LVCMOS33 } [get_ports { RESET }];
#IO_L3P_T0_DQS_AD1P_15 Sch=cpu_resetrn

##Pmod Header JB
set_property -dict { PACKAGE_PIN D14 IOSTANDARD LVCMOS33 } [get_ports { R_cmd }];
#IO_L1P_T0_AD0P_15 Sch=jb[1]

#set_property -dict { PACKAGE_PIN F16 IOSTANDARD LVCMOS33 } [get_ports { JB[2] }];
#IO_L14N_T2_SRCC_15 Sch=jb[2]

set_property -dict { PACKAGE_PIN G16 IOSTANDARD LVCMOS33 } [get_ports { Mux_sel }];
#IO_L13N_T2_MRCC_15 Sch=jb[3]

set_property -dict { PACKAGE_PIN H14 IOSTANDARD LVCMOS33 } [get_ports { CAS }];
#IO_L15P_T2_DQS_15 Sch=jb[4]

```

```

set_property -dict { PACKAGE_PIN E16 IOSTANDARD LVCMOS33 } [get_ports { RAS }];
#IO_L11N_T1_SRCC_15 Sch=jb[7]

set_property -dict { PACKAGE_PIN F13 IOSTANDARD LVCMOS33 } [get_ports { W }];
#IO_L5P_T0_AD9P_15 Sch=jb[8]

set_property -dict { PACKAGE_PIN H16 IOSTANDARD LVCMOS33 } [get_ports { clk }];
#IO_L13P_T2_MRCC_15 Sch=jb[10]

```

## Task Two

### Vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity readrcmd is
    Port (
        clk, R_cmd, RESET: in std_logic;
        Mux_sel, CAS, RAS, W: out std_logic
    );
end readrcmd;

architecture Behavioral of readrcmd is
    type state is (idle,s1,s2,s3,s4,s5,s6,s7,s8,s9,s10,s11,s12,s13,s14);
    signal present_state, next_state: state:= idle;
begin
    process(R_cmd, present_state)
    begin
        case present_state is
            when idle =>
                CAS <= '0';
                RAS <= '1';
                W <= '0';
                Mux_sel <= '0';
                if R_cmd = '1' then
                    next_state <= s1;
                else
                    next_state <= idle;
                end if;

            when s1 =>
                CAS <= '1';
                RAS <= '0';
                W <= '0';
                Mux_sel <= '0';
                next_state <= s2;

            when s2 =>
                CAS <= '1';
                RAS <= '0';
                W <= '0';
                Mux_sel <= '0';
                next_state <= s3;

            when s3 =>
                CAS <= '1';

```

```
RAS <= '0';
W <= '0';
Mux_sel <= '0';
next_state <= s4;

when s4 =>
Mux_sel <= '0';
CAS <= '1';
RAS <= '0';
W <= '0';
next_state <= s5;

when s5 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '0';
W <= '1';
next_state <= s6;

when s6 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s7;

when s7 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s8;

when s8 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s9;

when s9 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '1';
next_state <= s10;

when s10 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '0';
W <= '1';
next_state <= s11;

when s11 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
next_state <= s12;

when s12 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
next_state <= s13;

when s13 =>
Mux_sel <= '1';
CAS <= '1';
```

```

RAS <= '1';
W <= '1';
next_state <= s14;

when s14 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
if R_cmd = '1' then
    next_state <= s1;
else
    next_state <= idle;
end if;

when others =>
    next_state <= idle;

end case;
end process;

process
begin
wait until clk'event and clk = '1';
    if reset <= '0' then
        present_state <= idle;
    else
        present_state <= next_state;
    end if;
end process;

end Behavioral;

```

## Tcl

```

restart
add_force clk {0 0ns} {1 10ns} -repeat_every 20ns

add_force RESET {0 0ns}
run 20ns
add_force RESET {1 0ns}
run 20ns
add_force W_cmd {1 0ns}
run 300ns

```

## Xdc

```

## Clock signal
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk]

#set_property -dict { PACKAGE_PIN E3 IOSTANDARD LVCMOS33 } [get_ports { CLK100MHZ }];
#IO_L12P_T1_MRCC_35 Sch=clk100mhz

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK100MHZ}];

##Buttons
set_property -dict { PACKAGE_PIN C12 IOSTANDARD LVCMOS33 } [get_ports { RESET }];
#IO_L3P_T0_DQS_AD1P_15 Sch=cpu_resetrn

##Pmod Header JB
#set_property -dict { PACKAGE_PIN D14 IOSTANDARD LVCMOS33 } [get_ports { JB[1] }];
#IO_L1P_T0_AD0P_15 Sch=jb[1]

set_property -dict { PACKAGE_PIN F16 IOSTANDARD LVCMOS33 } [get_ports { W_cmd }];
#IO_L14N_T2_SRCC_15 Sch=jb[2]

```

```

set_property -dict { PACKAGE_PIN G16 IOSTANDARD LVCMOS33 } [get_ports { Mux_sel }];
#IO_L13N_T2_MRCC_15 Sch=jb[3]

set_property -dict { PACKAGE_PIN H14 IOSTANDARD LVCMOS33 } [get_ports { CAS }];
#IO_L15P_T2_DQS_15 Sch=jb[4]

set_property -dict { PACKAGE_PIN E16 IOSTANDARD LVCMOS33 } [get_ports { RAS }];
#IO_L11N_T1_SRCC_15 Sch=jb[7]

set_property -dict { PACKAGE_PIN F13 IOSTANDARD LVCMOS33 } [get_ports { W }];
#IO_L5P_T0_AD9P_15 Sch=jb[8]

set_property -dict { PACKAGE_PIN H16 IOSTANDARD LVCMOS33 } [get_ports { clk }];
#IO_L13P_T2_MRCC_15 Sch=jb[10]

```

## Task Three

vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity rwcmd is
    Port (
        R_cmd, W_cmd, RESET, clk: in std_logic;
        Mux_sel, CAS, RAS, W: out std_logic
    );
end rwcmd;

architecture Behavioral of rwcmd is
    type state is (s1, s2, s3, s4, s5, s6, s7, s8, s9, s10, s11, s12, s13, s14, s15, s16, s17);
    signal present_state, next_state: state:=s1;
    begin
        process(R_cmd, W_cmd, present_state)
        begin
            case present_state is

                when s1 =>
                    Mux_sel <= '0';
                    CAS <= '0';
                    RAS <= '1';
                    W <= '1';
                    if R_cmd = '1' and W_cmd = '0' then
                        next_state <= s2;
                    elsif R_cmd = '0' and W_cmd = '1' then
                        next_state <= s2;
                    elsif R_cmd = '0' and W_cmd = '0' then
                        next_state <= s1;
                    else
                        next_state <= s2;
                    end if;

                when s2 =>
                    Mux_sel <= '0';
                    CAS <= '1';
                    RAS <= '0';
                    W <= '1';
                    if R_cmd = '1' and W_cmd = '0' then
                        next_state <= s3;

```

```

elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s3;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s3 =>
Mux_sel <= '0';
CAS <= '1';
RAS <= '0';
W <= '1';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s4;
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s4;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s4 =>
Mux_sel <= '0';
CAS <= '1';
RAS <= '0';
W <= '1';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s5;
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s5;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s5 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '0';
W <= '0';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s6;
    W <= '0';
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s6;
    W <= '0';
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s6 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '0';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s7;
    W <= '1';
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s7;
    W <= '0';
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

```



```

when s7 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s8;
    W <= '1';
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s8;
    W <= '0';
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s8 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '0';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s9;
    W <= '1';
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s9;
    W <= '0';
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s9 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '0';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s10;
    W <= '1';
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s10;
    W <= '0';
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s10 =>
Mux_sel <= '1';
CAS <= '0';
RAS <= '0';
W <= '0';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s11;
    W <= '1';
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s11;
    W <= '0';
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s11 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '0';

```

```

if R_cmd = '1' and W_cmd = '0' then
    next_state <= s12;
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s12;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s12 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s13;
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s13;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s13 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s14;
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s14;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s14 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s15;
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s15;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when s15 =>
Mux_sel <= '1';
CAS <= '1';
RAS <= '1';
W <= '1';
if R_cmd = '1' and W_cmd = '0' then
    next_state <= s2;
elsif R_cmd = '0' and W_cmd = '1' then
    next_state <= s2;
elsif R_cmd = '0' and W_cmd = '0' then
    next_state <= s1;
else
    next_state <= s2;
end if;

when others =>

```

```

        next_state <= s1;

end case;
end process;

process
begin
wait until clk'event and clk = '1';
if reset = '0' then
    present_state <= s1;
else
    present_state <= next_state;
end if;
end process;

end Behavioral;

```

## tcl

```

restart
add_force clk {0 0ns} {1 10ns} -repeat_every 20ns

add_force RESET {0 0ns}
run 20ns
add_force RESET {1 0ns}
run 20ns
add_force R_cmd {1 0ns}
add_force W_cmd {1 0ns}
run 160ns
add_force R_cmd {0 0ns}
run 50ns
add_force W_cmd {0 0ns}
run 20ns

```

## xdc

```

## Clock signal
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk]
set_property -dict { PACKAGE_PIN E3 IOSTANDARD LVCMOS33 } [get_ports { CLK100MHZ }];
#IO_L12P_T1_MRCC_35 Sch=clk100mhz

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK100MHZ}];

##Buttons
set_property -dict { PACKAGE_PIN C12 IOSTANDARD LVCMOS33 } [get_ports { RESET }];
#IO_L3P_T0_DQS_AD1P_15 Sch=cpu_resetrn

##Pmod Headers
##Pmod Header JB
set_property -dict { PACKAGE_PIN D14 IOSTANDARD LVCMOS33 } [get_ports { R_cmd }];
#IO_L1P_T0_AD0P_15 Sch=jb[1]

set_property -dict { PACKAGE_PIN F16 IOSTANDARD LVCMOS33 } [get_ports { W_cmd }];
#IO_L14N_T2_SRCC_15 Sch=jb[2]

set_property -dict { PACKAGE_PIN G16 IOSTANDARD LVCMOS33 } [get_ports { Mux_sel }];
#IO_L13N_T2_MRCC_15 Sch=jb[3]

set_property -dict { PACKAGE_PIN H14 IOSTANDARD LVCMOS33 } [get_ports { CAS }];
#IO_L15P_T2_DQS_15 Sch=jb[4]

set_property -dict { PACKAGE_PIN E16 IOSTANDARD LVCMOS33 } [get_ports { RAS }];
#IO_L11N_T1_SRCC_15 Sch=jb[7]

```

```
set_property -dict { PACKAGE_PIN F13 IOSTANDARD LVCMOS33 } [get_ports { W }];  
#IO_L5P_T0_AD9P_15 Sch=jb[8]  
  
set_property -dict { PACKAGE_PIN H16 IOSTANDARD LVCMOS33 } [get_ports { clk }];  
#IO_L13P_T2_MRCC_15 Sch=jb[10]
```